

UNIVERSITÉ LIBRE DE BRUXELLES
ECOLE POLYTECHNIQUE DE BRUXELLES



ECOLE
POLYTECHNIQUE
DE BRUXELLES

MECA-H312 : Power Electronics - Practical Work sessions

Simulations :

Buck and Boost converters (ideal components)

PART 2

Rapport rendu le 25 février 2021

GROUPE 6

Étudiants

BAULER Thomas
OCHEA Emma
SAIDI Biyoha-Bintis
SAISON Arnaud
URY Ewald

Assistante

GUENAOU Jihad

Professeur

GYSELINCK Johan

Année académique 2020-2021

MATLAB files and data

All MATLAB files and data are available on this group's GitHub page : https://github.com/ArnautSaison/Power_Electronics_ELEC-H312_groupe6/tree/main/SimBB-Buck%20and%20Boost%20converters.

1. Buck (with ideal components)

1.4 Discontinuous conduction mode (DCM)

a) We set the resistance at $40\ \Omega$ which gives Figure 1.1.

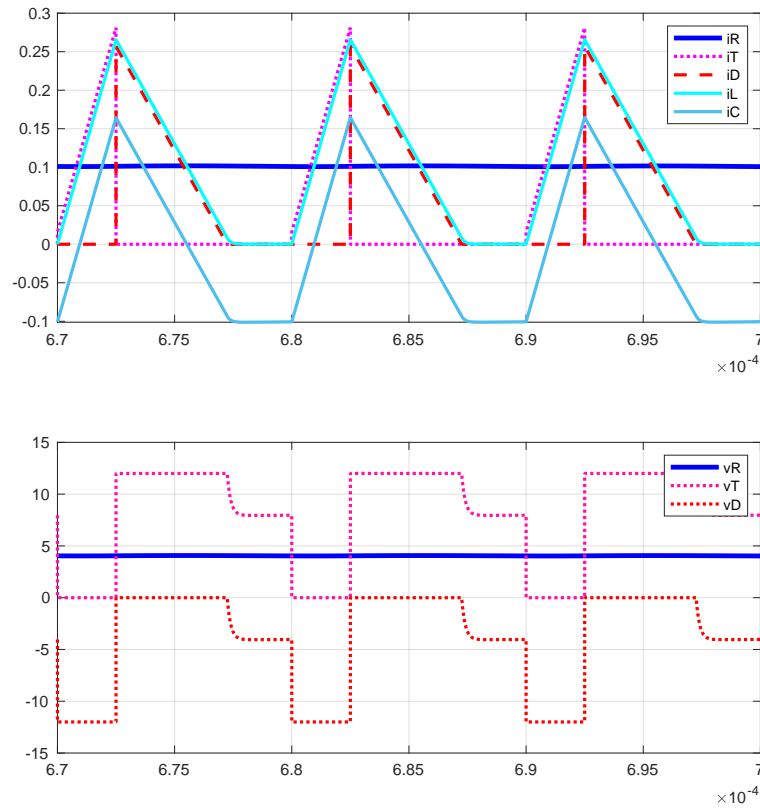


FIGURE 1.1 – Result with $40\ \Omega$ load resistance

Thanks to the *Mean* block and a *Display*, we measure $I_R = 0.1012\text{ A}$. This value can then be plugged into Equations 1.1 and 1.2. **The computed average output voltage V_R** is consistent with the measured average = 4.049 V (same method as for I_R).

$$V_R = \frac{D^2}{\left(D^2 + \frac{1}{4} * I_R / I_{Rref}\right)} * V_I = 3.9683\text{ V} \quad (1.1)$$

$$I_{Rref} = \frac{V_I}{8 * L * f_s} \quad (1.2)$$

The **peak inductor current I_{Lmax}** is analytically computed with Equation 1.3 and corresponds to the experimental value of 0.26 A.

$$I_{Lmax} = D * (V_i - V_R) * \left(\frac{1}{L}\right) * \frac{1}{f_s} = 0.2677 \text{ A} \quad (1.3)$$

The **fraction of non-conduction characterized by Δ_1 and Δ_2** is computed with equations 1.4 and 5 and approximately corresponds to the experimental values $\Delta_{1exp} = 4.8e - 6 * f_s = 0.48$ and $\Delta_{2exp} = 2.7e - 6 * f_s = 0.27$.

$$\Delta_1 = D * \left(\frac{V_i - V_O}{V_R}\right) = 0.5060 \quad (1.4)$$

$$\Delta_2 = 1 - D - \Delta_1 = 0.2440 \quad (1.5)$$

- b) Figure 1.2 shows the results for $R = 200 \Omega$. These results correspond to the analytical values (see Table 1.1).
- c) Figure 1.2 shows the results for $R = 2000 \Omega$. The seems to be an error in the simulation, generating values with up to an order of magnitude difference (see Table 1.1).

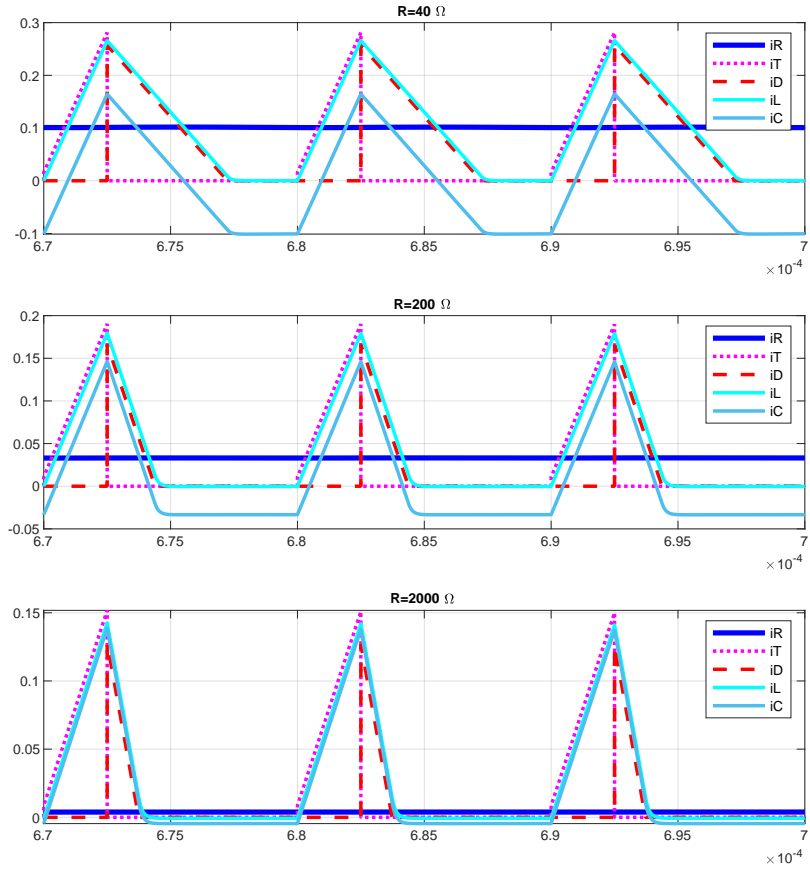


FIGURE 1.2 – Result with 40 Ω , 200 Ω and 2000 Ω load resistances

Load resistance	40 Ω	200 Ω	2000 Ω
V_R	3.9683	7.2141	11.1357
$V_{R \text{ exp}}$	4.049	6.634	7.776 ?
I_{Lmax}	0.2677	0.1595	0.0288
$I_{Lmax \text{ exp}}$	0.26	0.18	0.1466 ?
Δ_1	0.5060	0.1658	0.0194
$\Delta_1 \text{ exp}$	0.48	$\approx 20\%$	$\approx 10\%$?
Δ_2	0.2440	0.5842	0.7306
$\Delta_2 \text{ exp}$	0.27	$\approx 60\%$	$\approx 70\%$

TABLE 1.1 – Comparison of output variables for different load resistances

1.5 More steady-state current and voltages waveform (CCM and DCM)

a) See Figure 1.3.

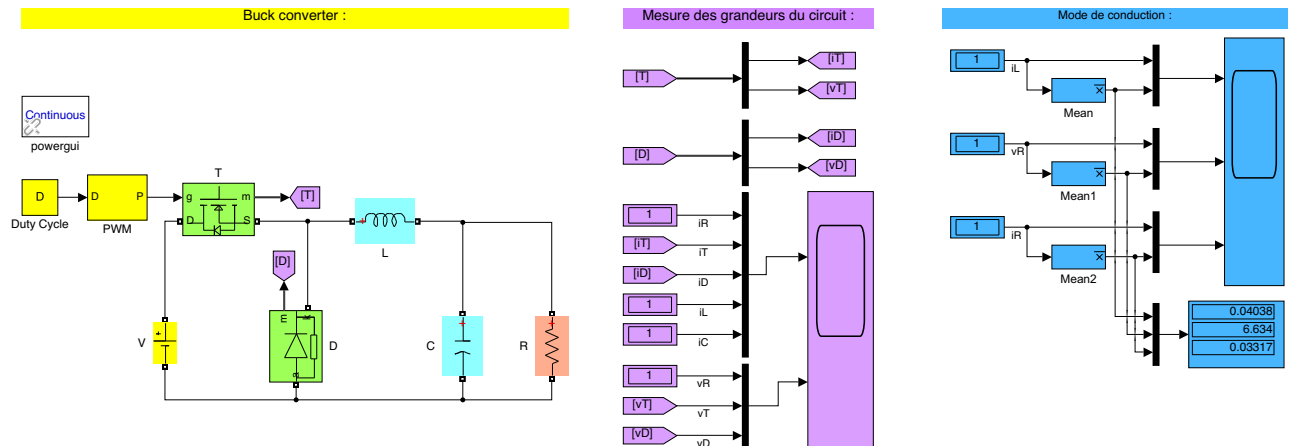


FIGURE 1.3 – Full Simulink model

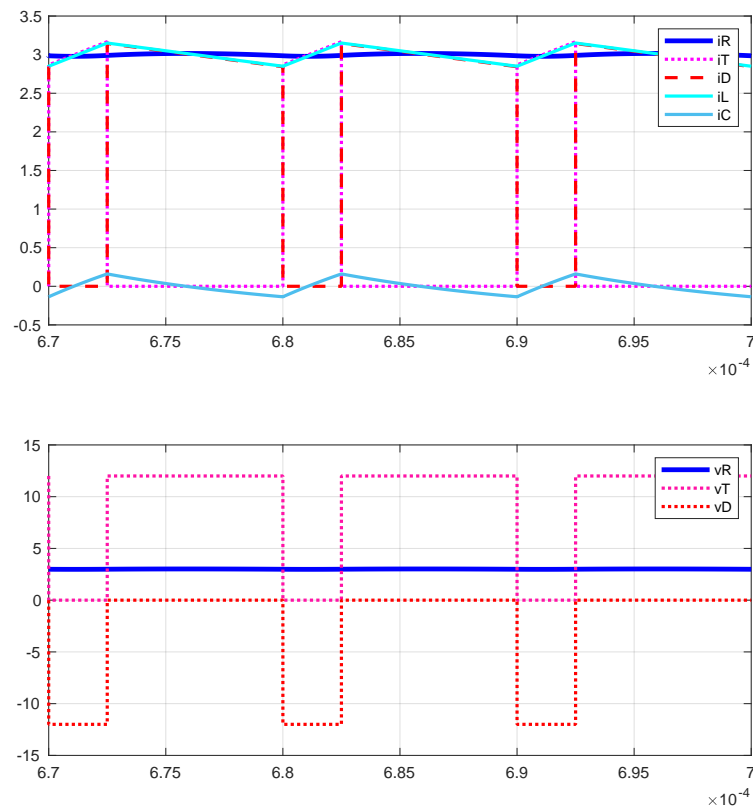


FIGURE 1.4 – Simulation with 1 Ω load resistance : CCM

b)

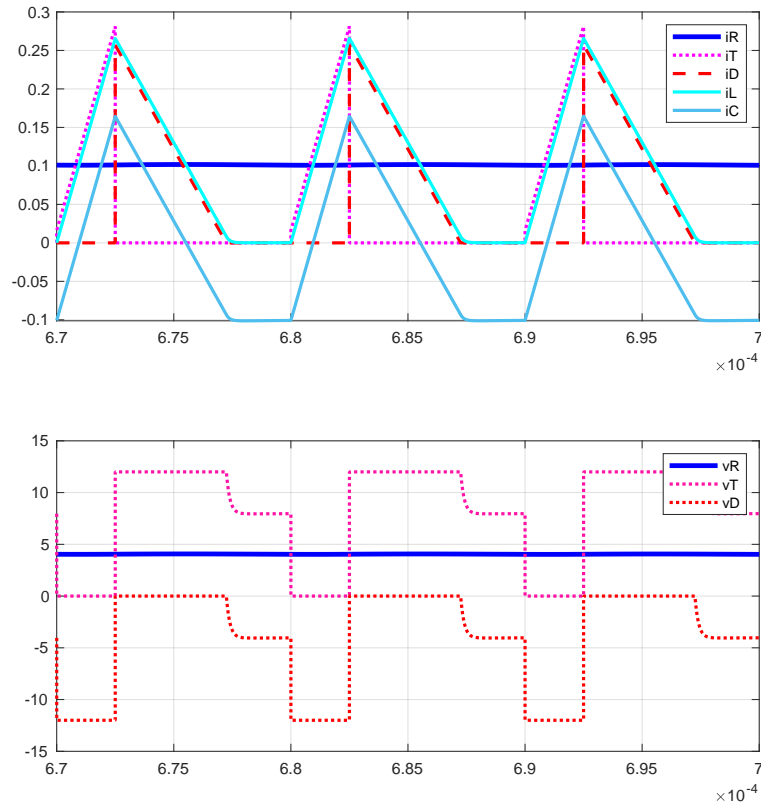


FIGURE 1.5 – Simulation with $40 \, \Omega$ load resistance : DCM

c)

1.6 Complete output-voltage-current curve with a MATLAB script

The script below gives us multiple output-voltage-current curves depending on the duty cycle. Each curve follows a variation of the load resistance with an imposed duty cycle. Figure 1.6 shows the different curves, appearing as a function of the duty cycle. The script allows us to calculate the output current and voltage that are respectively the x-axis and the y-axis (see GitHub link).

As the Figure 1.6 shows, for a short value of resistance, we are in a continuous conduction mode and as the resistance grows, we tend to zero output current normalized and enter the discontinuous conduction mode.

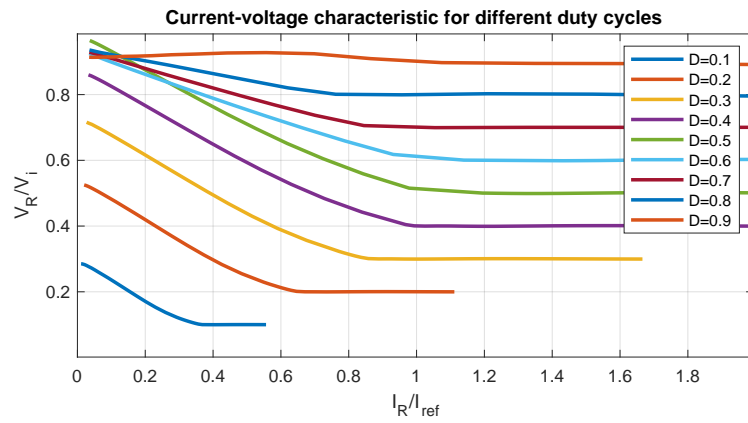


FIGURE 1.6 – Multiple output-voltage-current curves

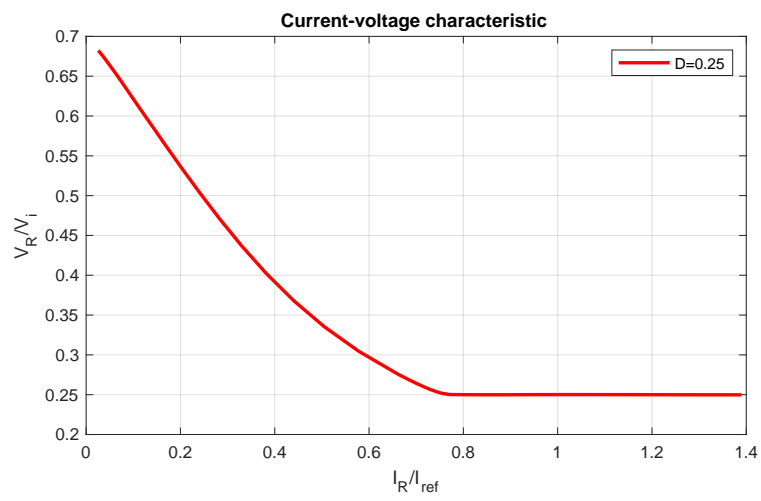


FIGURE 1.7 – Current-voltage characteristic for duty cycle of 0.25

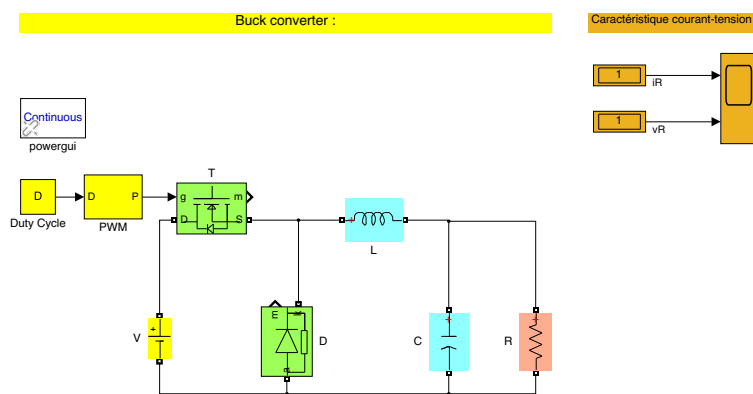


FIGURE 1.8 – Simplified model used to compute the current-voltage characteristics